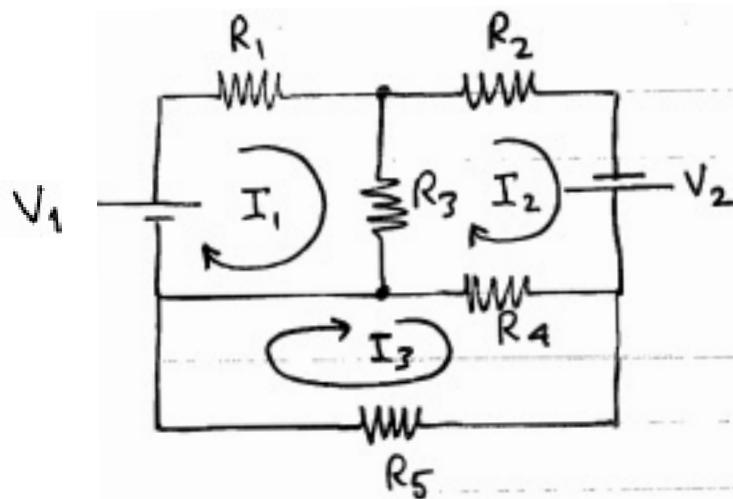


1

Solución del Parcial.

1.-

Malla 1:

$$V_1 - I_1 R_1 - I_1 R_3 + I_2 R_3 = 0$$

$$V_1 - I_1 (R_1 + R_3) + I_2 R_3 = 0$$

$$V_1 = I_1 (R_1 + R_3) - I_2 R_3$$

Malla 2:

$$V_2 - I_2 R_4 - I_2 R_3 - I_2 R_2 + I_1 R_3 + I_3 R_4 = 0$$

$$V_2 - I_2 (R_4 + R_3 + R_2) + I_1 R_3 + I_3 R_4 = 0$$

$$V_2 = -I_1 R_3 + I_2 (R_4 + R_3 + R_2) - I_3 R_4$$

Malla 3:

$$-I_3 R_4 - I_3 R_5 + I_2 R_4 = 0$$

$$-I_3 (R_4 + R_5) + I_2 R_4 = 0$$

$$-I_2 R_4 + I_3 (R_4 + R_5) = 0$$

$$\begin{bmatrix} V_1 \\ V_2 \\ 0 \end{bmatrix} = \begin{bmatrix} R_1 + R_3 & -R_3 & 0 \\ -R_3 & R_4 + R_3 + R_2 & -R_4 \\ 0 & -R_4 & R_4 + R_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} 10V \\ 20V \\ 0 \end{bmatrix} = \begin{bmatrix} 7K_2 & -2K_2 & 0 \\ -2K_2 & 9K_2 & -4K_2 \\ 0 & -4K_2 & 6K_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

Resolviendo el sistema de ecuaciones

$$I_1 = 2.58 \text{ mA}$$

$$I_2 = 3.98 \text{ mA}$$

$$I_3 = 2.67 \text{ mA}$$

Elemento	Potencia
V ₁	+25.8 mW
V ₂	+79.6 mW
R ₁	-33.28 mW
R ₂	-47.52 mW
R ₃	-3.92 mW
R ₄	-6.86 mW
R ₅	-14.26 mW


+ ≡ "Potencia Entregada"
 - ≡ "Potencia Disipada"

Balanzo de Potencia (Redondeando de cimales)

$$26 \text{ mW} + 80 \text{ mW} = 33 \text{ mW} + 48 \text{ mW} + 4 \text{ mW} + 7 \text{ mW} + 14 \text{ mW}$$

$$106 \text{ mW} = 106 \text{ mW}$$


2.

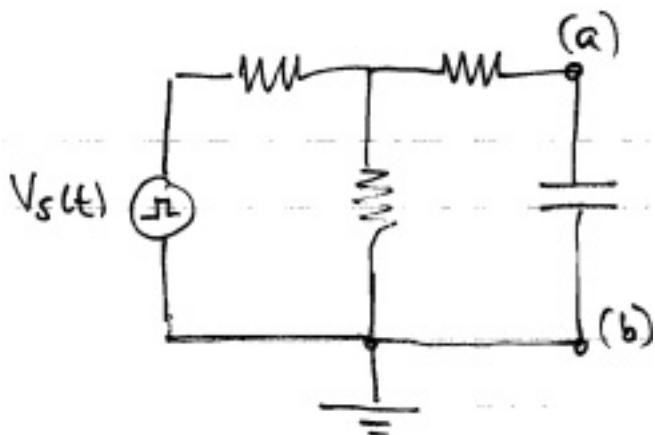

Simplificamos el circuito utilizando Thévenin.


Circuito de

Carga

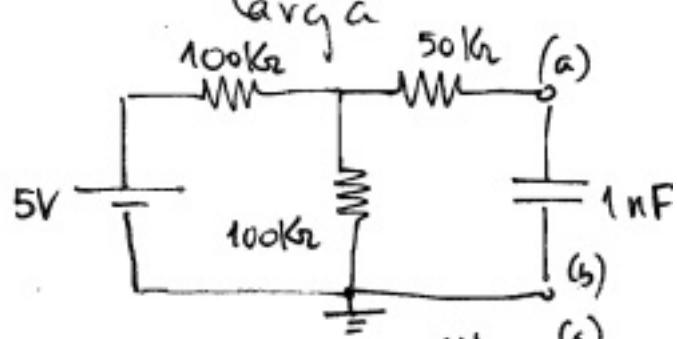



Circuito de

Descarga

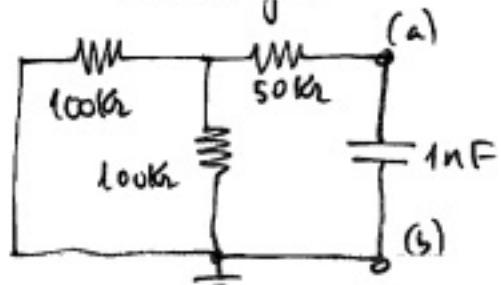



Circuito de

Línea

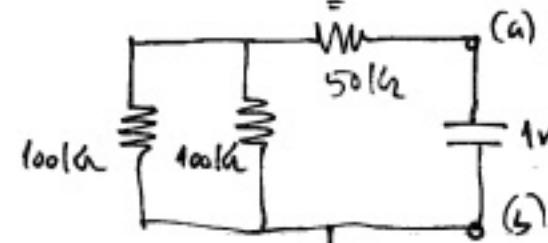
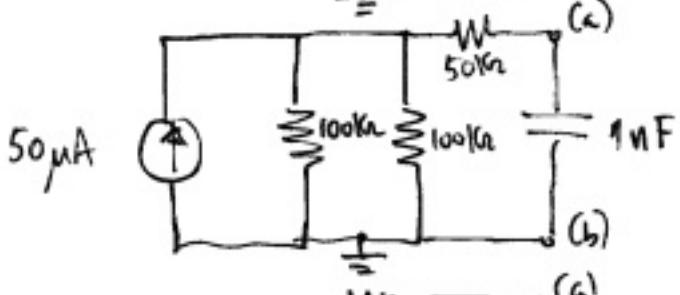


Circuito de

Alimentación

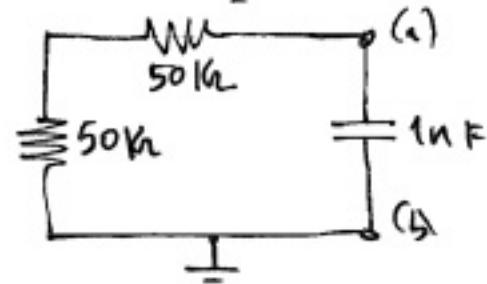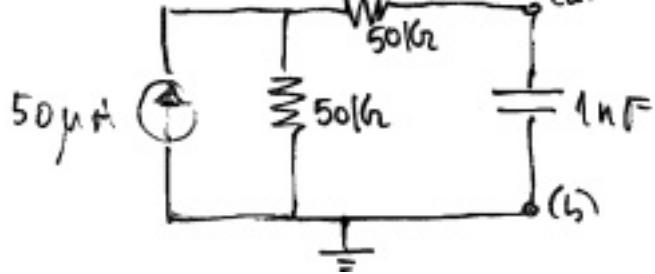


4

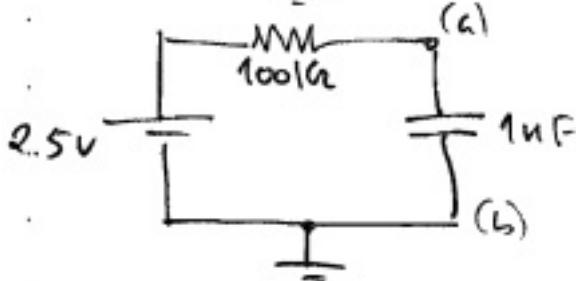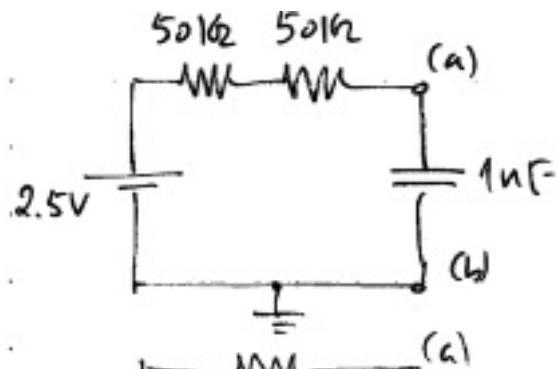

$$V_c(t) = E \left(1 - e^{-t/\tau_{RC}}\right)$$
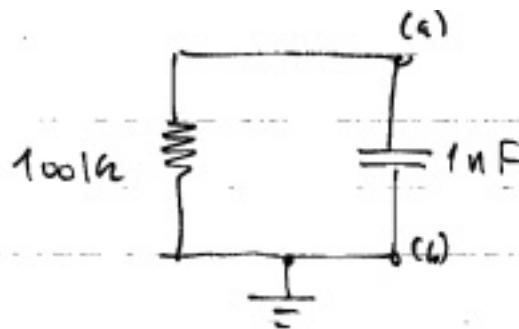
$$I_c(t) = \frac{E}{R} e^{-t/\tau_{RC}}$$



$$V_c(t) = E e^{-t/\tau_{RC}}$$

$$I_c(t) = -\frac{E}{R} e^{-t/\tau_{RC}}$$

$\langle S \rangle$	$\langle V \rangle$	$\langle I_A \rangle$	$\langle V \rangle$	$\langle I_A \rangle$
t	V_c	I_c	V_c	I_c

t	V_c	I_c	V_c	I_c
1τ	1.58	9.2	0.92	-9.2
2τ	2.16	3.4	0.34	-3.4
3τ	2.38	1.2	0.12	-1.2
4τ	2.45	0.5	0.05	-0.5
5τ	2.48	0.2	0.02	-0.2



carga

descarga






$$f = 1 \text{ KHz} \Rightarrow T = 1 \text{ ms} \Rightarrow T/2 = 500 \mu\text{s}$$

$$\tau = RC \Rightarrow \tau = 100 \mu\text{s} \Rightarrow 5\tau = 500 \mu\text{s}$$


Pregunta 2

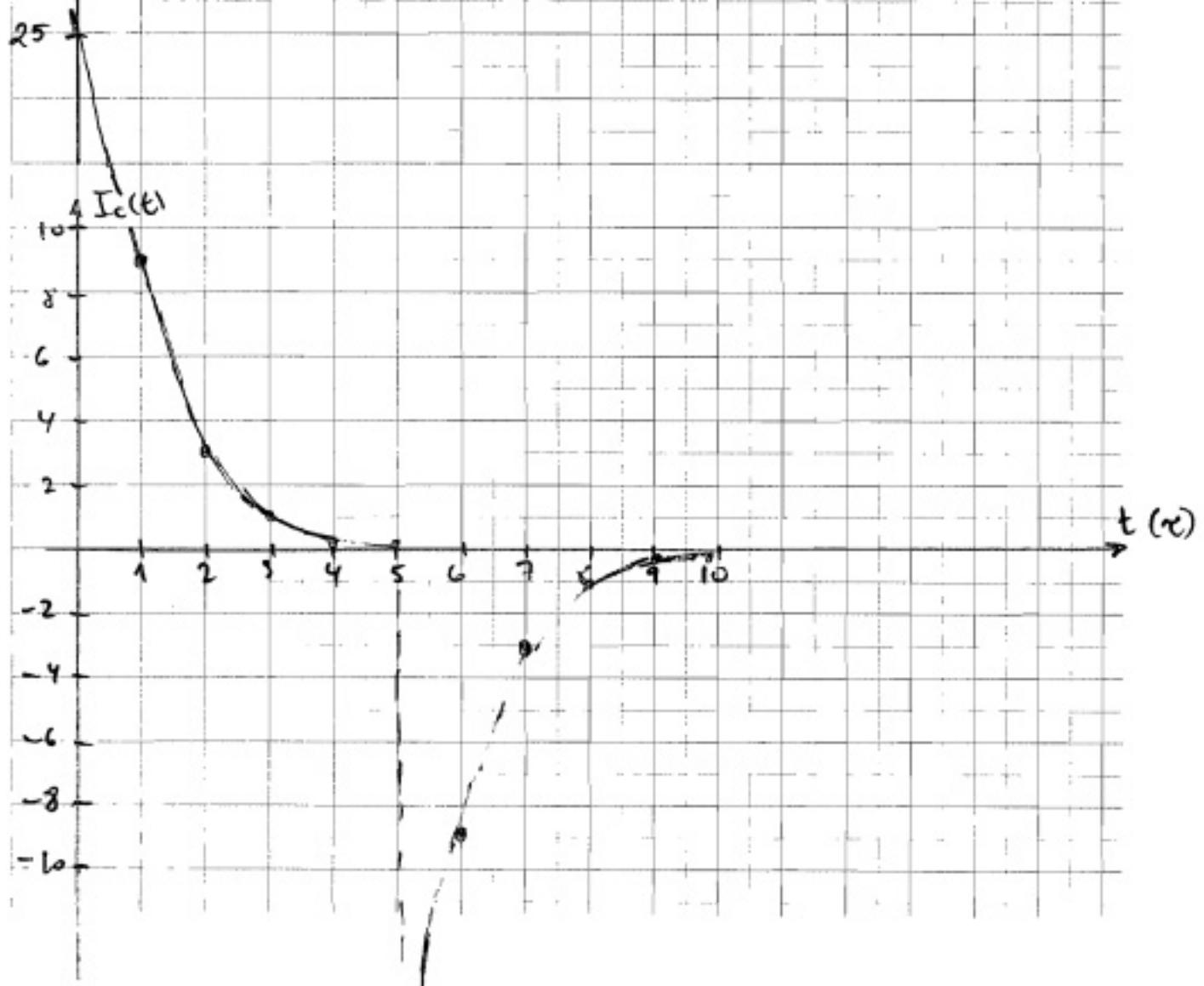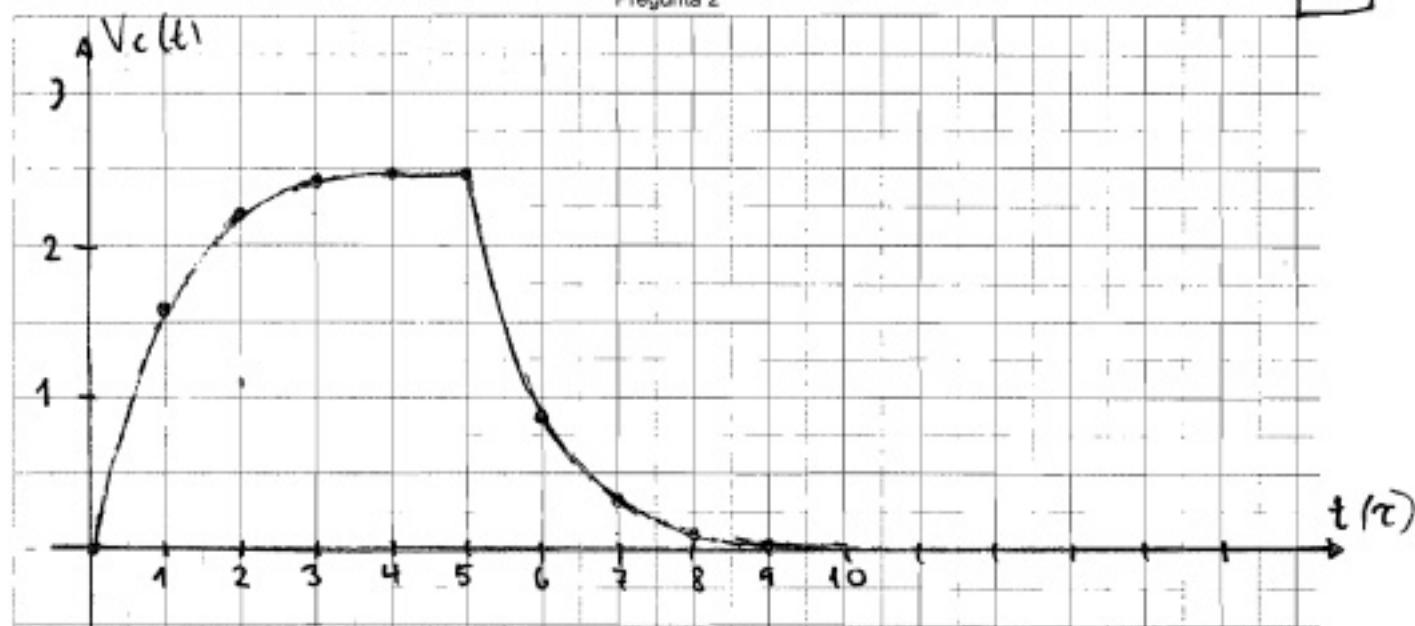

3.-

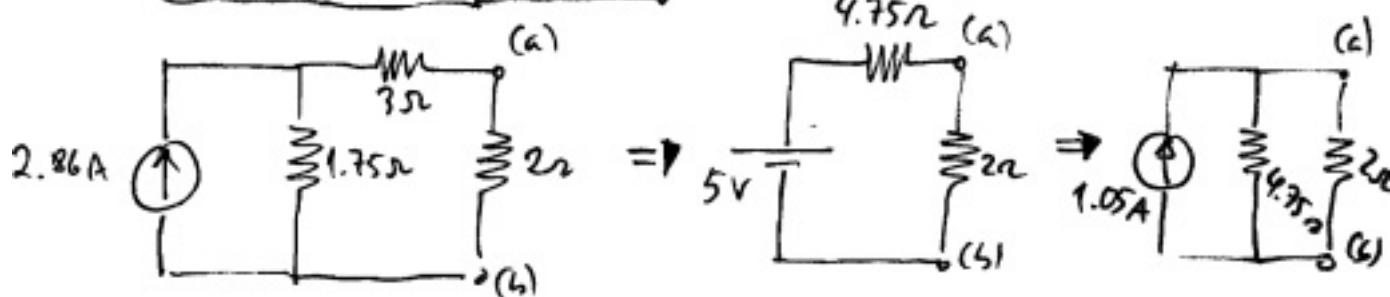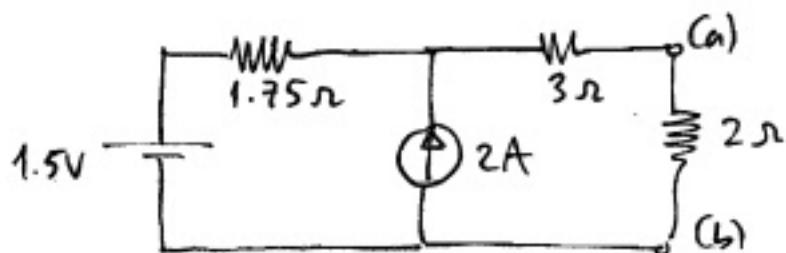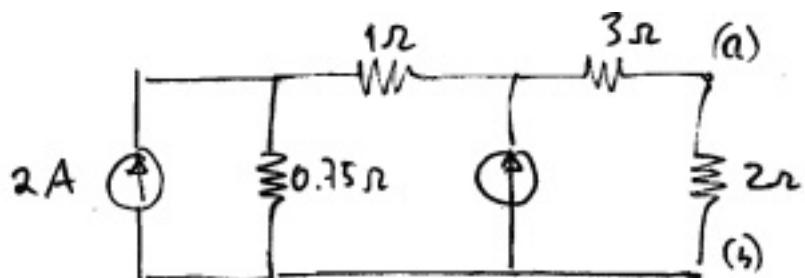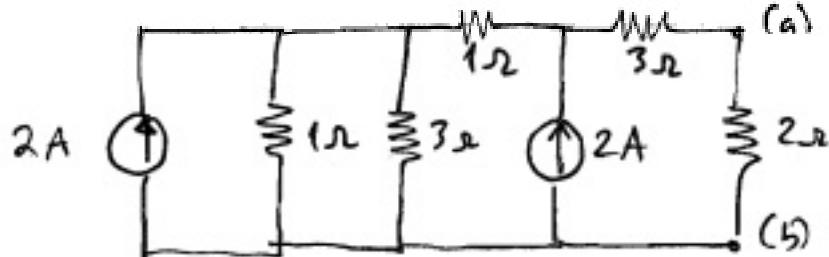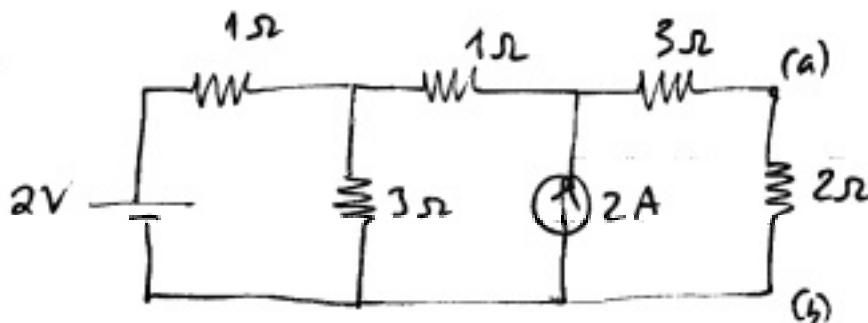

7

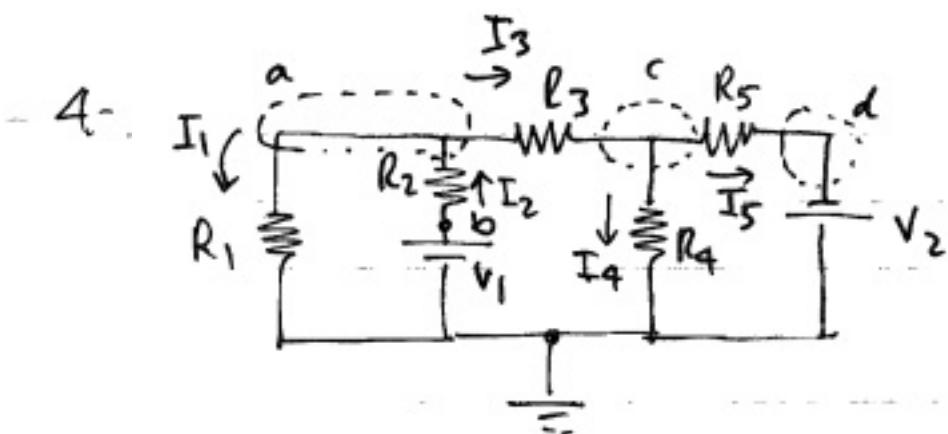

$$I_1 = \frac{V_a}{R_1}$$

$$\frac{V_1 - V_a}{R_2} = \frac{V_a}{R_1} + \frac{V_a - V_c}{R_3}$$

$$I_2 = \frac{V_b - V_a}{R_2}$$

$$\frac{V_1}{R_2} = \frac{V_a}{R_1} + \frac{V_a}{R_2} + \frac{V_a}{R_3} - \frac{V_c}{R_3}$$

$$I_3 = \frac{V_a - V_c}{R_3}$$

(I)

$$\frac{V_1}{R_2} = V_a \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{V_c}{R_3}$$

$$I_4 = \frac{V_c}{R_4}$$

$$\frac{V_a - V_c}{R_3} = \frac{V_c}{R_4} + \frac{V_c + V_2}{R_5}$$

$$I_5 = \frac{V_c - V_d}{R_5}$$

$$\frac{V_a}{R_3} - \frac{V_c}{R_3} = \frac{V_c}{R_4} + \frac{V_c}{R_5} + \frac{V_2}{R_5}$$

$$V_b = V_1$$

$$V_d = -V_2$$

$$(II) \quad \frac{V_2}{R_5} = \frac{V_a}{R_3} - V_c \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right)$$

$$I_2 = I_1 + I_3$$

$$(I) \quad 5A = V_a \frac{8}{10} - \frac{V_c}{10}$$

$$I_3 = I_4 + I_5$$

$$(II) \quad 25A = \frac{V_a}{10} - V_c \frac{68}{80}$$

[8]

$$V_a = 2.61 \text{ V}$$

$$V_b = -29.1 \text{ V}$$

$$I_1 = 1.30 \text{ A}$$

$$I_2 = 10.45 \text{ A}$$

$$I_3 = 3.17 \text{ A}$$