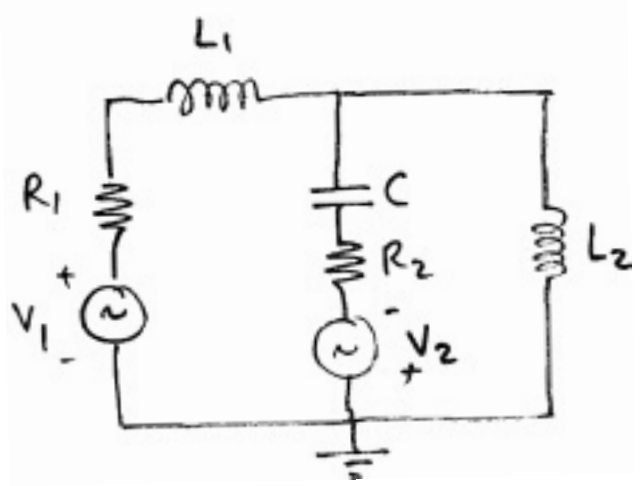


Solución

1.-




- Aplicamos Malla (más usado)

$$Z_1 = R_1 + jX_{L1}$$

$$Z_2 = R_2 - jX_{C1}$$

$$Z_3 = jX_{L2}$$

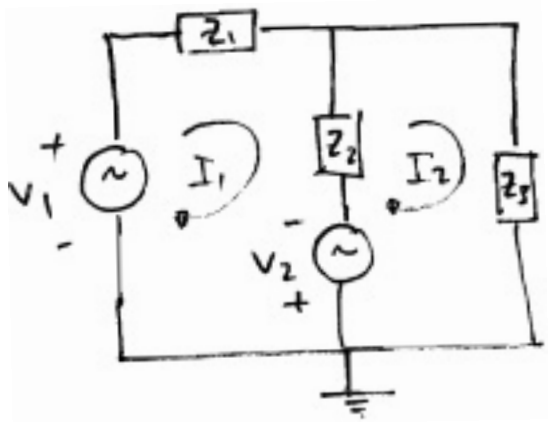

$$Z_1 = 1\Omega + j2\Omega$$

$$Z_2 = 4\Omega - j8\Omega$$

$$Z_3 = j6\Omega$$

Malla 1:

$$V_1 - I_1 Z_1 - I_1 Z_2 + V_2 + I_2 Z_2 = 0$$

$$V_1 + V_2 - I_1 (Z_1 + Z_2) + I_2 Z_2 = 0$$

$$V_1 + V_2 = I_1 (Z_1 + Z_2) - I_2 Z_2 \quad (I)$$

Malla 2:

$$-V_2 - I_2 Z_2 - I_2 Z_3 + I_1 Z_2 = 0$$

$$-V_2 - I_2 (Z_2 + Z_3) + I_1 Z_2 = 0$$

$$-V_2 = I_2 (Z_2 + Z_3) - I_1 Z_2 \quad (II)$$

$$\begin{bmatrix} V_1 + V_2 \\ -V_2 \end{bmatrix} = \begin{bmatrix} z_1 + z_2 & -z_2 \\ -z_2 & z_2 + z_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_1 = \frac{\begin{bmatrix} V_1 + V_2 & -z_2 \\ -V_2 & z_2 + z_3 \end{bmatrix}}{\begin{bmatrix} z_1 + z_2 & -z_2 \\ -z_2 & z_2 + z_3 \end{bmatrix}}$$

$$I_1 = \frac{(V_1 + V_2)(z_2 + z_3) - (-z_2)(-V_2)}{(z_1 + z_2)(z_2 + z_3) - (-z_2)(-z_2)}$$


$$I_1 = \frac{60.58 \angle 28.3}{63.53 \angle 28.1} = 0.95 \angle 0.2^\circ < A >$$

$$I_2 = \frac{\begin{bmatrix} z_1 + z_2 & V_1 + V_2 \\ -z_2 & -V_2 \end{bmatrix}}{\begin{bmatrix} z_1 + z_2 & -z_2 \\ -z_2 & z_2 + z_3 \end{bmatrix}}$$

$$I_2 = \frac{(z_1 + z_2)(-V_2) - (V_1 + V_2)(-z_2)}{(z_1 + z_2)(z_2 + z_3) - (-z_2)(-z_2)} = \frac{80.95 \angle -58.7}{63.53 \angle 28.2}$$

$$I_2 = 1.3 \text{ A } \angle -87^\circ$$

2.-

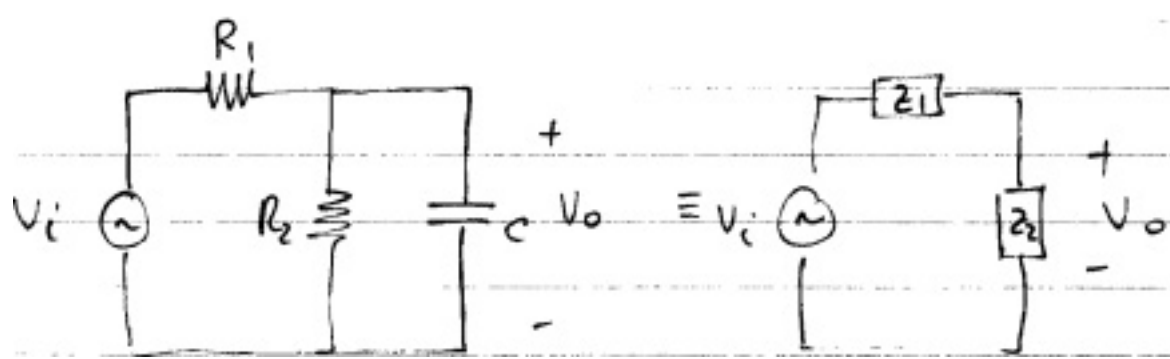

Por divisor de tensión:

$$V_o = V_i \frac{Z_2}{Z_1 + Z_2} \Rightarrow \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = R_1$$

$$Z_2 = R_2 \parallel \left(\frac{1}{j\omega C}\right)$$

$$\frac{V_o}{V_i} = \frac{R_2 \parallel \left(\frac{1}{j\omega C}\right)}{R_1 + R_2 \parallel \left(\frac{1}{j\omega C}\right)} = \frac{\frac{R_2 \left(\frac{1}{j\omega C}\right)}{R_2 + \frac{1}{j\omega C}}}{R_1 + \frac{R_2 \left(\frac{1}{j\omega C}\right)}{R_2 + \frac{1}{j\omega C}}}$$

$$\frac{V_o}{V_i} = \frac{\frac{R_2}{R_2 j\omega C + 1}}{R_1 + \frac{R_2}{R_2 j\omega C + 1}} = \frac{R_2}{R_1 (R_2 j\omega C + 1) + R_2}$$

$$\boxed{\frac{V_o}{V_i} = \frac{1}{j R_1 \omega C + 2}}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{(R_1 \omega C)^2 + 2^2}}$$



$$\omega \rightarrow 0 \Rightarrow \left| \frac{V_o}{V_i} \right| \approx 0.5$$

$$\omega \rightarrow \infty \Rightarrow \left| \frac{V_o}{V_i} \right| \approx 0$$

Filtro
Pasa bajas

ω	$\left \frac{V_o}{V_i} \right $
1	0.49
10	0.45
20	0.35
30	0.28
40	0.22
50	0.18
60	0.16
70	0.13
80	0.12
90	0.11
100	0.10

3.-

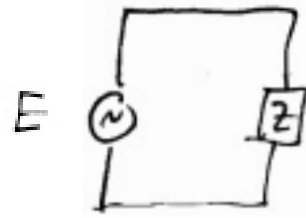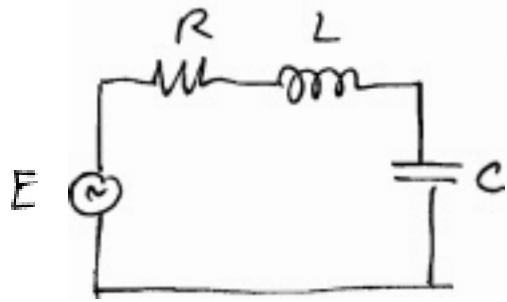

$$I = \frac{E}{Z}$$

$$Z = R + jX_L - jX_C$$

$$I = \frac{100V \angle 0^\circ}{6\Omega + j7\Omega - j15\Omega} = \frac{100V \angle 0^\circ}{10\Omega \angle -53.13^\circ}$$

$$i = 10A \angle 53.13^\circ \leftarrow \text{ángulo entre } V \text{ e } I$$

$$P = U \cdot I \cos \alpha = (100V) (10A) \cos(53.17^\circ)$$


$$P = 600W \leftarrow \text{Potencia disipada}$$

$$Q = VI \sin \theta = (100V) (10A) \sin(53.13^\circ)$$


$$Q = 800VAR \leftarrow \text{Potencia reactiva}$$

$$S = V \cdot I = (100V) (10A) = 1000V \cdot A$$

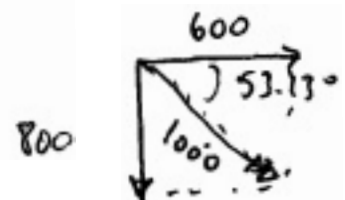
$$F.P. = \frac{P}{S} = \frac{600W}{1000VA} = 0.6$$



4.-

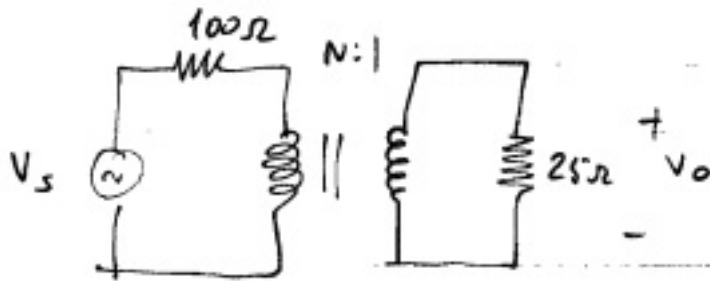

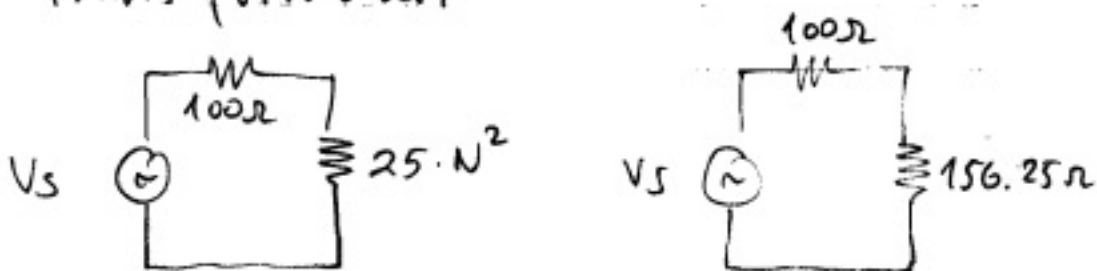Reflejando hacia el primario del transformador



$$i_s = \frac{V_s}{100 + 156.25\Omega} = \frac{294 \cos(377t)}{256.25\Omega}$$

$$i_s = 1.15 \text{ A } \cos(377t)$$

Reflejando hacia el secundario del transformador



Aplicamos divisor de tensión

$$V_o = \frac{V_s}{N} \frac{25\Omega}{25\Omega + \frac{100\Omega}{N^2}} = 117.6 \cos(377t) \frac{25\Omega}{25\Omega + 16\Omega}$$

$$V_o = 71.7 \cos(377t)$$